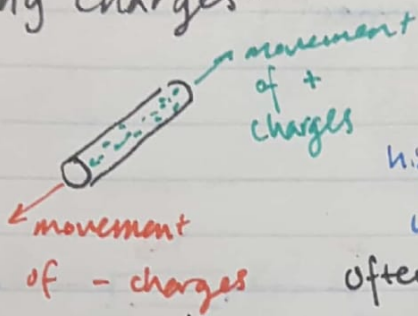


ECE 140

Current:

Jan 4, 2018

Moving charges.




$$i(t) = \frac{dq(t)}{dt} \leftarrow \text{charge in coulomb (C)}$$

high school way $\int = \frac{Q}{t}$ in Aps

often need to assume direction.

Reference Direction:

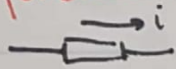


if $i +$, flows \rightarrow
else, flows \leftarrow

charge:


$$q(t) = q(t_0) + \int_{t_0}^t i(\tau) d\tau$$

Types of Current:

1) DC - constant wrt time.

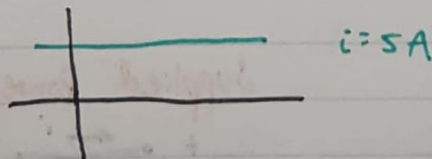

2) AC - sinusoidal

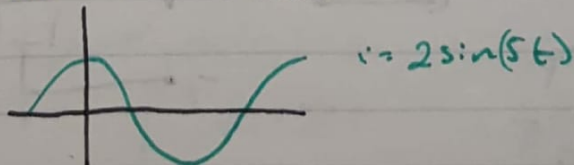




3) Time Varying:

ANYTHING BUT
AC / DC

$$i = 5e^{-2t}$$

Voltage:
 $V(t) = \frac{dW(t)}{dq}$ ← Energy (J)
 AKA emf, PD ← charge in Coulombs (C)
(E/Q from high school)

Example:

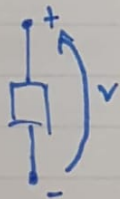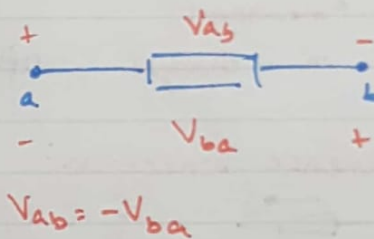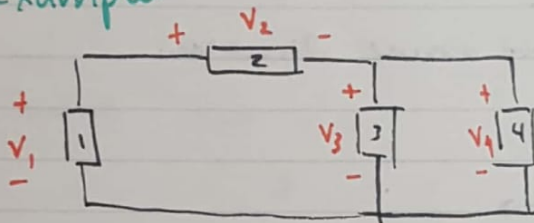

Also sometimes used.

Power:


$$p(t) = \frac{dW}{dt} \leftarrow \text{J} = \frac{dW}{dq} \cdot \frac{dq}{dt} = v \cdot i$$

↑
watts

Jan 8, 2018


Absorbed Power:

Current
+ → -
of v

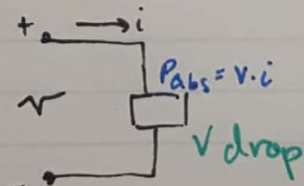

$$P_{abs} = -P_{sup}$$


Supplied Power:

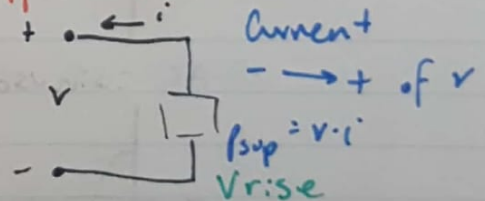

Passive sign convention ↑
 + → i → -

If $P_{abs} > 0$, actually absorbed. < 0 supplied.

Example:

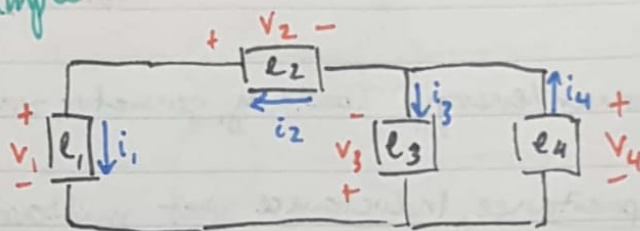

$$\begin{aligned} i_1 = i_2 = 5A & \quad V_1 = 8V \\ i_3 = -2A & \quad V_2 = -2V \quad V_4 = 10V \\ i_4 = 3A & \quad V_3 = -10V \end{aligned}$$

a) Power for e_1 ? Not specified! Assume abs.

$$P_{abs} = V_1 i_1 = 40W \quad +40, \text{ so actually abs.}$$

b) P_{abs} for e_2 ?

$$P_{abs} = -V_2 i_2 = 10W \quad +10, \text{ so actually abs.}$$

c) P_{sup} for e_3 ?

$$P_{sup} = V_3 i_3 = 20W \quad +20, \text{ so actually sup.}$$

d) P_{abs} for e_4 ?

$$P_{abs} = -V_4 i_4 = -30W \quad -30, \text{ so actually sup.}$$

consumed

Conservation of Power/Energy:

$$\sum P_{abs} = \sum P_{sup} \quad \sum P = 0$$

Energy:

$$w = w(t_2) - w(t_1) = \int_{t_1}^{t_2} P(\tau) d\tau \quad \left\{ \text{number} \right\}$$

Assume $t_1 = -\infty, w(t_1) = 0$.

$$w(t) = \int_{-\infty}^t P(\tau) d\tau \quad \left\{ \text{function of } t. \right\}$$

Circuit Elements:

Jan 9, 2018

1) Active:

↳ Generates power/energy (battery, generator, transistor)


2) Passive:

↳ Resistance, Capacitance, Inductance post midterm.

↳ Absorbs / stores energy.

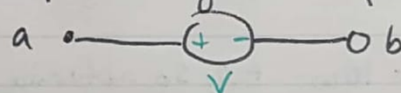3) Independent Voltage Source:


↳ Specific v regardless of i . (Not constant, but independent)



$V_{ab} = V$, no matter i

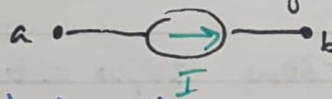
4) Independent Current Source:

↳ Specific current regardless of v . (" ")



5) Dependent Sources:

a) Voltage-controlled Voltage Source:

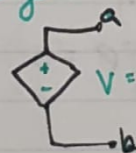


$V = \alpha V_x$ α : constant.

control V .

V_x somewhere in rest of circuit.

b) Current-controlled Voltage Source:

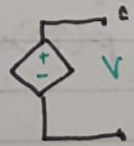


$V = r \cdot i_x$

control current

Same deal


c) Current-controlled Current Source:

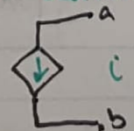

$i = \beta \cdot i_x$

Same

d) Voltage-controlled Current Source:

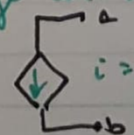


$i = g \cdot V_x$

Same

I, V
independent
of each other


Series Connection:

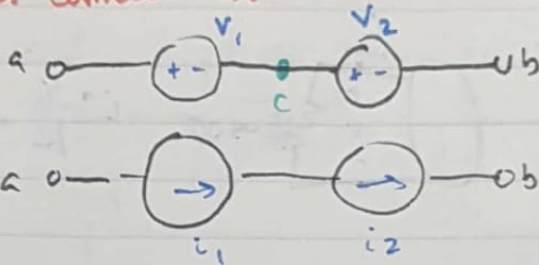


Only V_1, V_2 connected at c.

i_1 should = i_2 (else invalid)

Parallel connection:

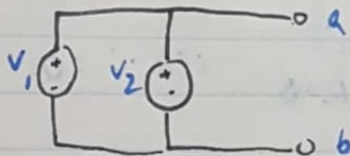


V_1 should = V_2
(else invalid)

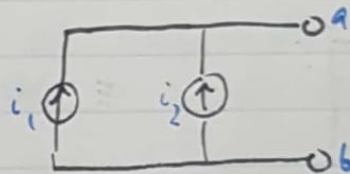

valid

"Parallel" - Connected btwn same two nodes (a, b).

Resistance and Ohm's Law:

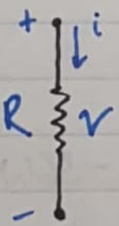

$$V = R \cdot i$$


$$R \geq 0$$

$$\hookrightarrow i = \frac{1}{R} \cdot V$$

$$= G \cdot V$$

where G = conductance in Siemens (or Ω^{-1})


Note:

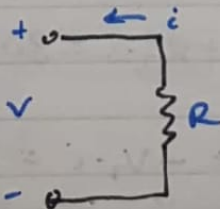

$$V = -R \cdot i \text{ for this}$$

(watch for current direction)

Power:

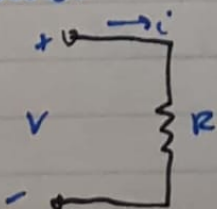

$$P_{abs} = V \cdot i$$

$$= R \cdot i^2$$



$$= \frac{V^2}{R}$$

≥ 0 b/c of $\frac{1}{2}$



resistors always absorb power.

Open Circuit:

Jan 10, 2018

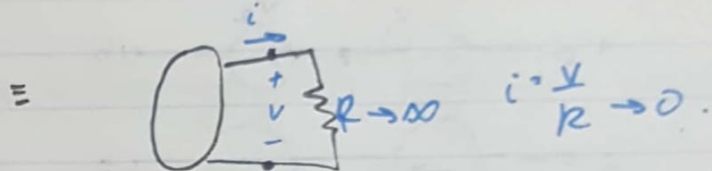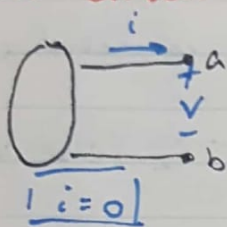


Short Circuit:

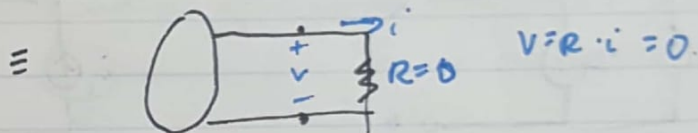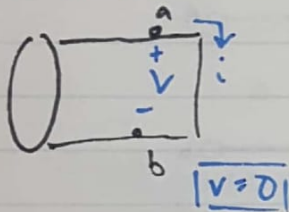

Example:

1)

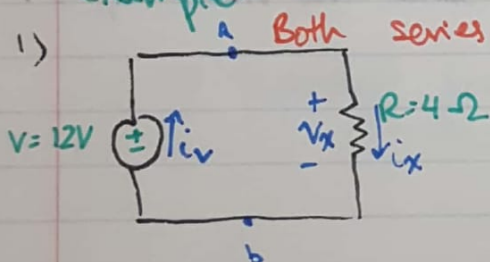


$$V_x = 12V \quad (-12V \text{ if } -+)$$

$$i_x = \frac{V_x}{R} = 3A$$

$$i_v = i_x = 3A$$

$$P_{R,abs} = 12 \cdot 3 = 36W \text{ and } P_{v,abs} = -V \cdot i = -36W$$

2)

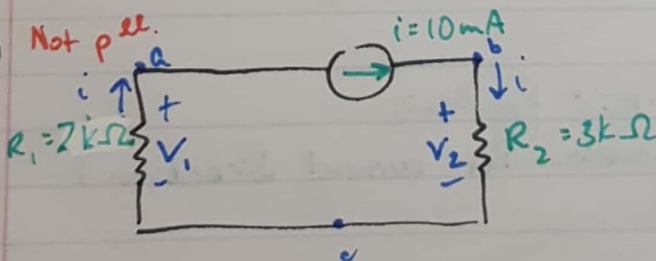

$$V_1 = -R_1 \cdot i = -20V$$

$$V_2 = R_2 \cdot i = 30V$$


$$P_{R1,abs} = -V_1 \cdot i = 200mW$$

$$P_{R2,abs} = V_2 \cdot i = 300mW$$

Kirchhoff's Current Law (KCL):

Jan 17, 2018

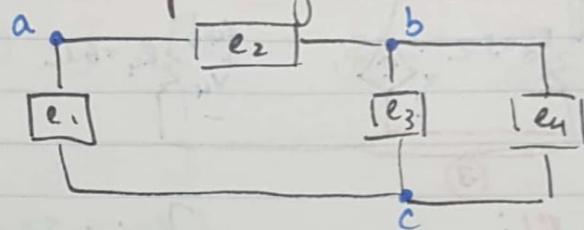A node: pt or junction where 2+ elements connected.




KCL: sum of all currents at any node = 0.

$$\sum_n i_n = 0$$

$i_{\text{enter}} = i_{\text{leaving node}}$

Example:

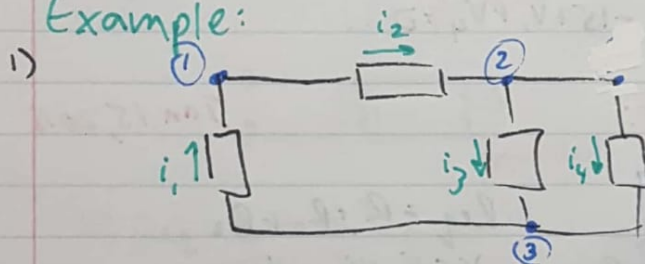

1) $i_1 = i_2$

2) $i_2 = i_3 + i_4$

3) $i_3 + i_4 = i_1$


Note lines - independence/dependence

N nodes give $N-1$ independent KCL eqn.

Kirchhoff's Voltage Law (KVL):

A loop: closed path where no element is encountered more than once.

mesh:
loop w/o any
loops inside it.

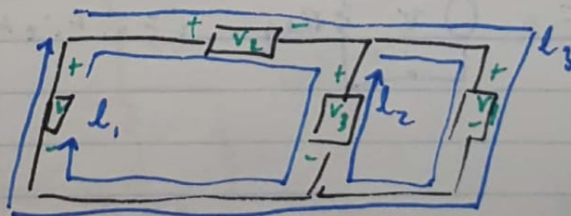

1) $V_1 = V_2 + V_3$

2) $V_3 = V_4$

3) $V_2 + V_4 = V_1$


KVL: sum of all voltages around any loop is 0.

$$\sum_n V_n = 0$$

$V_{\text{drops}} = V_{\text{rises}}$

N meshes give N independent KVL eqn.

Example:

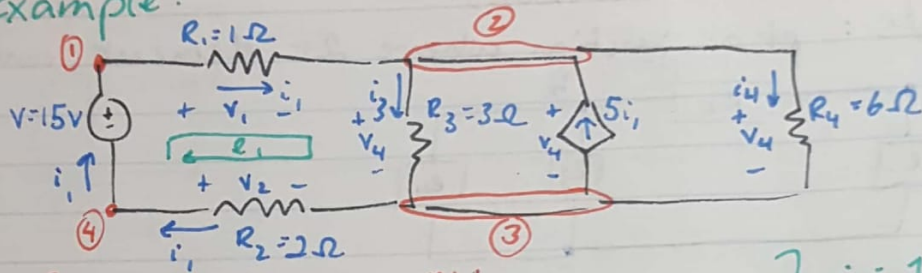

OL:

$$\begin{aligned} V_1 &= R_1 i_1 \\ V_2 &= -R_2 i_1 \\ V_4 &= R_3 i_3 \\ V_4 &= R_4 i_4 \end{aligned}$$

KCL:

Only need node 2


$$i_1 + 5i_1 = i_3 + i_4$$

KVL: Only need l_1

$$-V_2 - 15 + V_1 + V_4 = 0$$

$$\left. \begin{aligned} i_1 &= 1A & V_1 &= 1V \\ i_4 &= 2A & V_2 &= -2V \\ i_3 &= 4A & V_4 &= 12V \end{aligned} \right\}$$


Equivalent series Resistors:

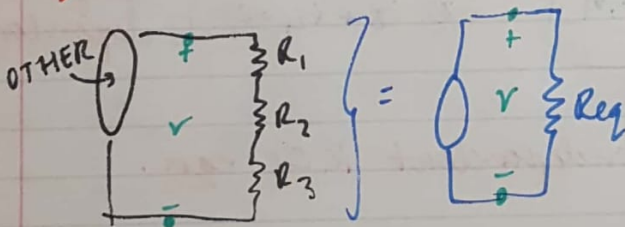

$$\begin{aligned} R_{eq} &= R_1 + R_2 + R_3 \\ V &= V_1 + V_2 + V_3 \end{aligned}$$


Jan 15, 2018


Equivalent Parallel Resistors:

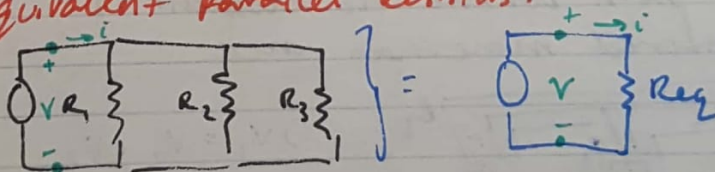

$$\begin{aligned} \frac{1}{R_{eq}} &= \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \\ i &= i_1 + i_2 + i_3 \end{aligned}$$


Note:

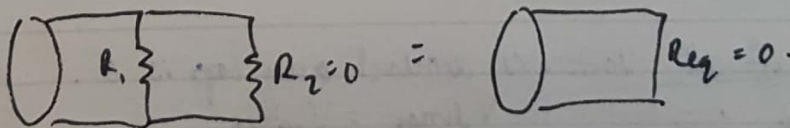

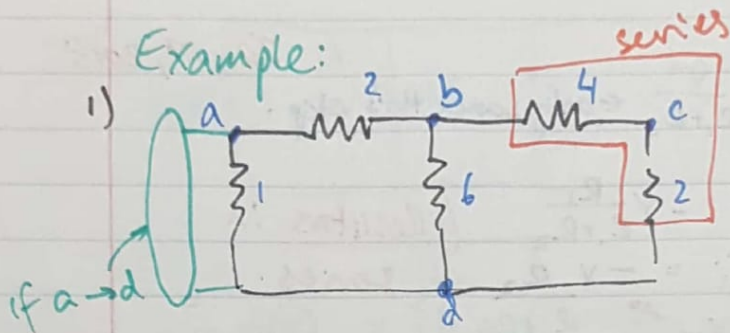


Should draw rest of circuit as left to show 1, 2 not in series.
 ↳ depends on nodes you want (a, d)



a) $R_{eq} A \rightarrow D$?

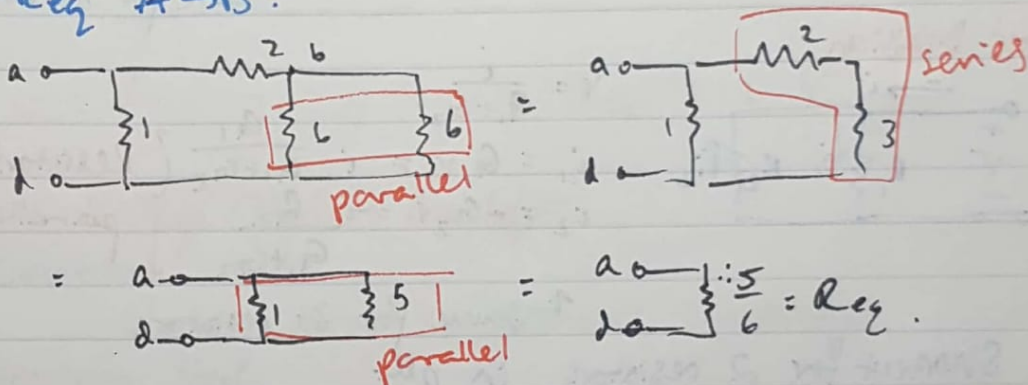

b) $R_{eq} B \rightarrow D$?

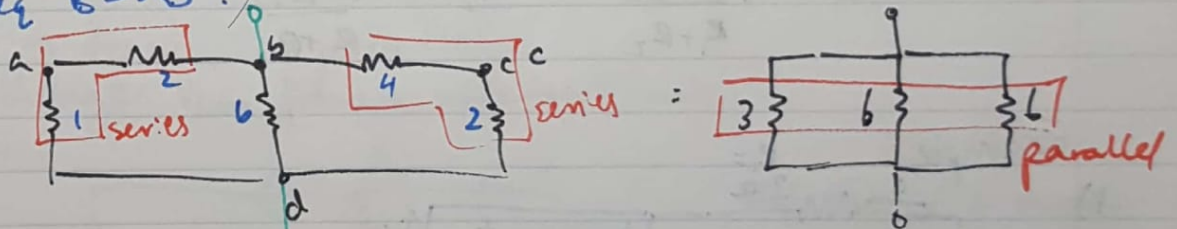


$\therefore R_{eq} = 1.5$

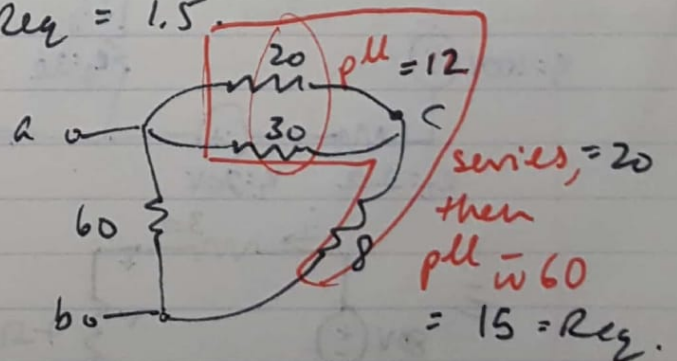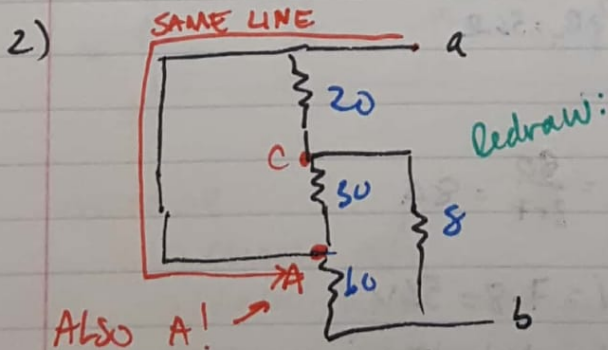

Voltage Division:

Jan 17, 2018

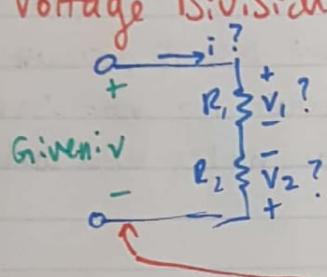

$$i = \frac{V}{R_1 + R_2} \leftarrow \text{only saves this step.}$$

$$V_1 = R_1 i = V \frac{R_1}{R_1 + R_2}$$


$$V_2 = -R_2 i = -V \frac{R_2}{R_1 + R_2}$$

based on $+V -$

Resistors in series.

Same for 3+ resistors

Current Division:

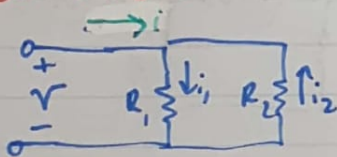

$$V = \frac{i}{G_1 + G_2}$$

$$i_1 = G_1 V = i \frac{G_1}{G_1 + G_2}$$

$$i_2 = -G_2 V = -i \frac{G_2}{G_1 + G_2}$$

Resistors in parallel

Same for 3+ resistors



Shortcut for 2 resistors in pll:

$$i_1 = i \frac{R_2}{R_1 + R_2}$$

$$i_2 = -i \frac{R_1}{R_1 + R_2}$$

Example:

1)

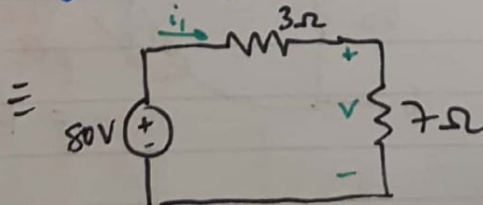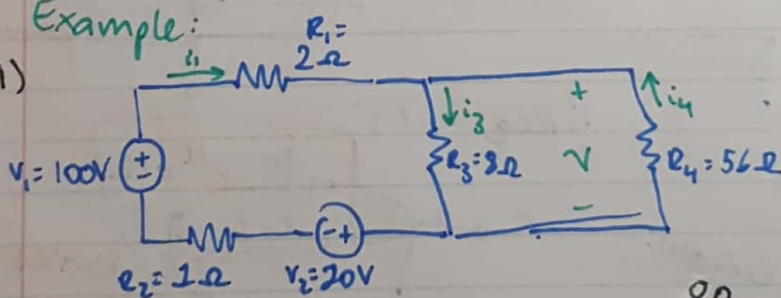

$$i_1 = \frac{80}{3+7} = 8A$$


$$V = 7 \cdot 8 = 56V$$

Now, just Ohm's law.

or, CD: $i_3 = i_1 \cdot \frac{R_4}{R_3 + R_4}$

$$i_4 = -i_1 \cdot \frac{R_3}{R_3 + R_4}$$

2)

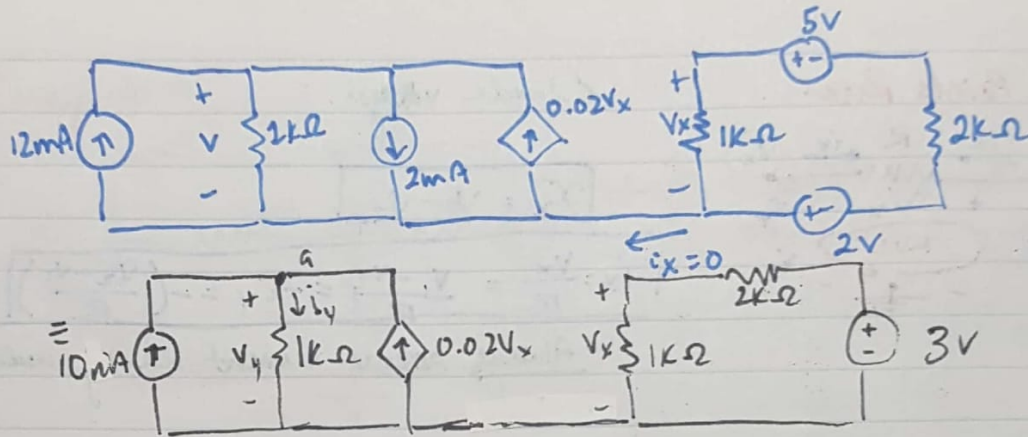

By VD: $V_x = 3 \cdot \frac{1}{1+2} = 1V$ Then KCL $V_y = 30V$

Nodal - Voltage (Nodal) Analysis:

Essential Node:

→ Node where 3+ elements connected.


Reference Node:

→ One of essential nodes chosen arb.

→ Assumed 0 potential.

Node Voltage: V_{node} from a node → ref. node.

Example:

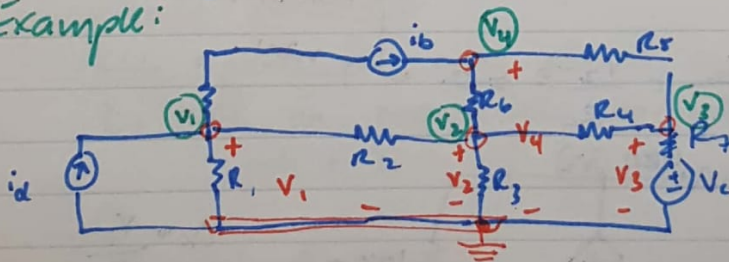


Jan 19, 2018

of node V's @ essential nodes = # of ind. eqns.
(4)

Procedure:

- 1) choose ref.
- 2) Label node voltages
- 3) Assign currents to branches (optional)
- 4) KCL at each non-ref essential node.
- 5) Ohm's law + KVL to get all I in terms of Voltages.

Three Points Rule:

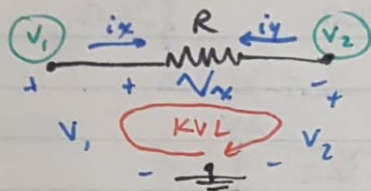


Node voltages.

$$V_x = V_1 - V_2$$

$$i_x = \frac{V_x}{R} = \frac{V_1 - V_2}{R} = -i_y = -\left(\frac{V_2 - V_1}{R}\right)$$

Always assume current leaving node

Example:

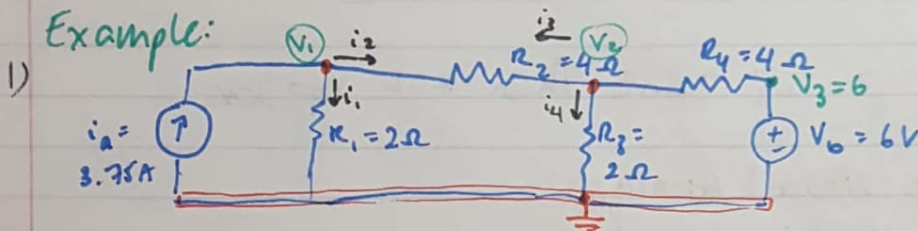

$$\text{KCL 1: } 3.75 = i_1 + i_2$$

$$i_1 + i_2 = -3.75 \quad \leftarrow \text{enter} = -ve, \text{leave} = +ve$$

$$\text{3pt rule: } \frac{V_1}{2} + \frac{V_1 - V_2}{4} = 3.75$$


$$0.75V_1 - 0.25V_2 = 3.75$$

$$\text{KCL 2:}$$

$$\frac{V_2 - V_1}{R_2} + \frac{V_2}{R_3} + \frac{V_2 - 6}{R_4} = 0$$

Can solve now.

2)

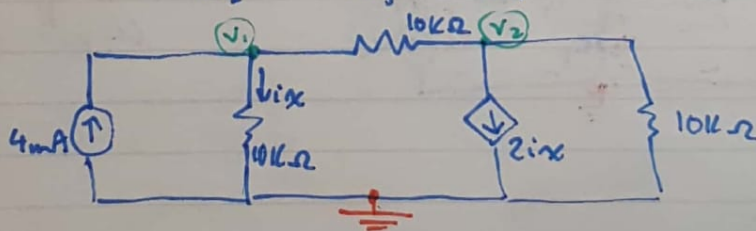

$$i_x = \frac{V_1}{10}$$

$$\text{KCL 1: } -4\text{mA} + \frac{V_1}{10\text{k}} + \frac{V_1 - V_2}{10\text{k}} = 0$$

$$\frac{2}{10}V_1 - \frac{1}{10}V_2 = 4$$

$$\text{KCL 2: } \frac{V_2 - V_1}{10} + 2i_x + \frac{V_2}{10} = 0$$

Solve.


$$V_1 = 16\text{V}$$

$$V_2 = -8\text{V}$$

Exceptions:

Jan 22, 2018

1)

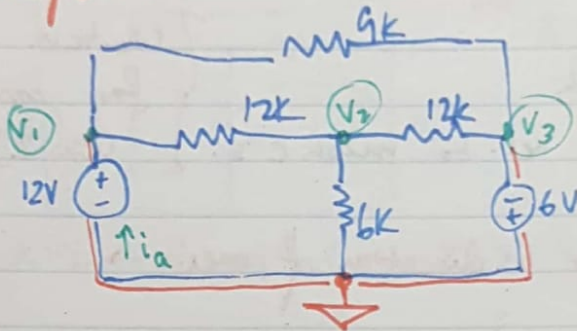


can't write current w/o resistance

$$V_1 = 12V \quad V_3 = -6V \text{ and KCL for 2} \\ V_2 = 1.5V$$

To get i_a , KCL V_1 :

$$i_a = \frac{V_1 - V_2}{12} + \frac{V_1 - V_3}{12} = 2.875 \text{ mA}$$

2)

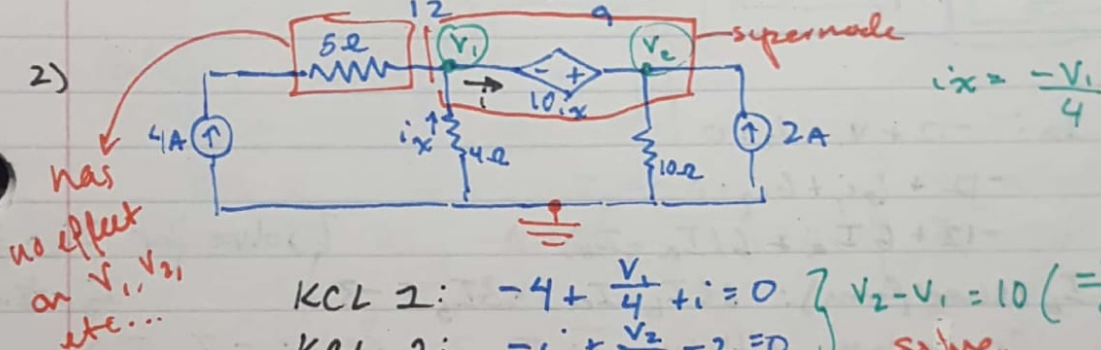

$$i_x = \frac{-V_1}{4}$$

$$\begin{aligned} \text{KCL 1: } -4 + \frac{V_1}{4} + i &= 0 \\ \text{KCL 2: } -i + \frac{V_2}{10} - 2 &= 0 \end{aligned} \quad \left. \begin{aligned} & \\ & \end{aligned} \right\} \begin{aligned} & V_2 - V_1 = 10 \left(\frac{-V_1}{4} \right) \text{ Now solve.} \end{aligned}$$

Supernode Shortcut:

KCL applies for any closed surface.

Do KCL on supernode to avoid using i .


$$-4 + \frac{V_1}{4} + \frac{V_2}{10} - 2 = 0$$

Mesh Current Analysis:

Jan 23, 2018

Mesh Current - Imaginary current, one direction + value.

Example:

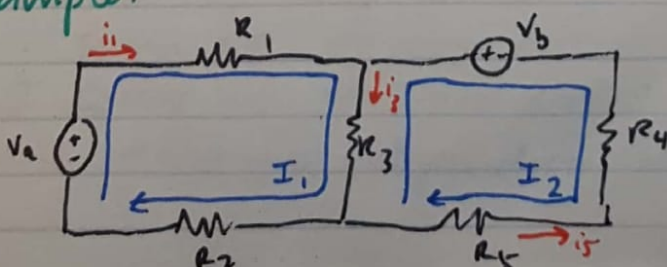


$$\begin{aligned} & I_1, I_2 \text{ mesh currents} \quad \text{branch currents} \\ & i_1 = I_1 \quad i_3 = I_1 - I_2 \quad i_2 = -I_2 \end{aligned}$$

Procedure:

- 1) Draw + label mesh c's
- 2) KVL around each mesh
- 3) O'L and KCL to get V rel. to mesh c's.

Watch for control (ex 2)

Example:

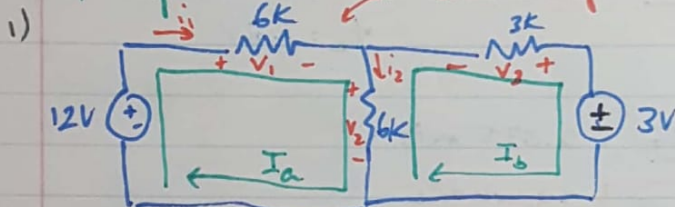

$$\text{KVL } I_a: -12 + V_1 + V_2 = 0$$

$$-12 + 6i_1 + 6i_2 = 0$$


$$-12 + 6I_a + 6(I_a - I_b) = 0$$

$$\text{KVL } I_b \text{ (short form)}: 6(I_b - I_a) + 3I_b = -3$$

solve for $I_a = \frac{5}{4} \text{ mA}$
 $I_b = \frac{1}{2} \text{ mA}$

Can solve either w/ I_b, I_a (ex: $i_2 = I_a - I_b$)

$$\Rightarrow V_3 = -3I_b$$

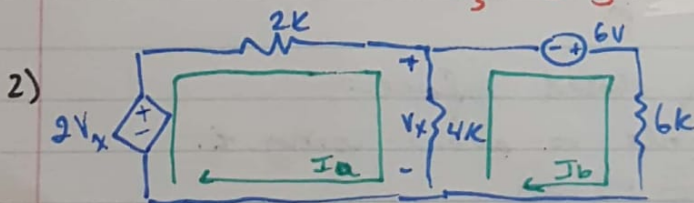


$$V_x = 4(I_a - I_b)$$

$$\text{KVL } I_a: -2V_x + 2I_a + V_x = 0$$

$$\text{KVL } I_b: 4(I_b - I_a) - 6 + 6I_b = 0$$


solve for $I_a = 6 \text{ mA}$
 $I_b = 3 \text{ mA}$

Jan 24, 2018

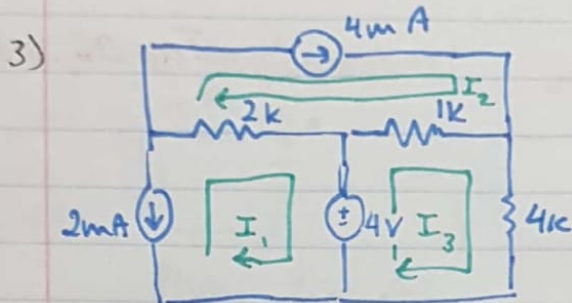

$I_1 = -2\text{mA}$
 $I_2 = 4\text{mA}$ } Don't need KVL for these.

KVL 3: $-4 + (I_3 - I_2) + 4I_3$

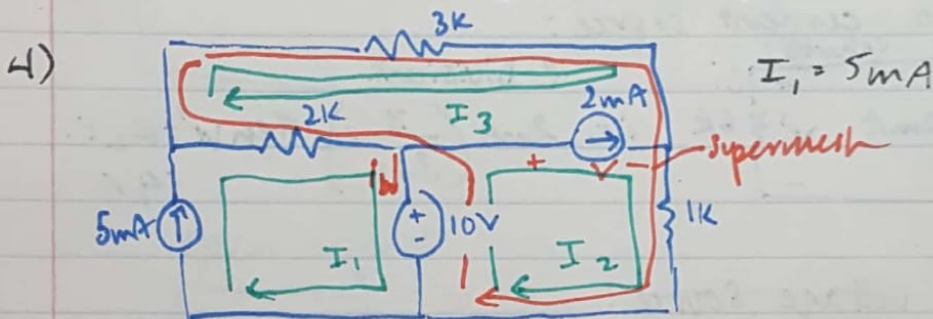

KVL 2: $-10 + V + I_2 = 0$

KVL 3: $3I_3 - V + 2(I_3 - I_1) = 0$

$I_2 - I_3 = 2$

$I_1 = 5\text{mA}$
 $I_2 = 5\text{mA}$
 $I_3 = 3\text{mA}$

Supermesh Shortcut:

KVL: $-10 + 2(I_3 - I_1) + 3I_3 + I_2 = 0$ (KVL 2 + KVL 3)

$i_b = I_1 - I_2 = 0 \Rightarrow$ removing this branch makes no diff.

Principle of Superposition:

Current/Voltage in a linear circuit can be found as the alg. sum of the indiv. contributions of each indep. source acting alone.

Deactivating Indep. Sources:


V source = 0. \Rightarrow short circuit.

I source = 0. \Rightarrow Open circuit.


*Not for dependent sources!!!!

Jan 26, 2018

Example:

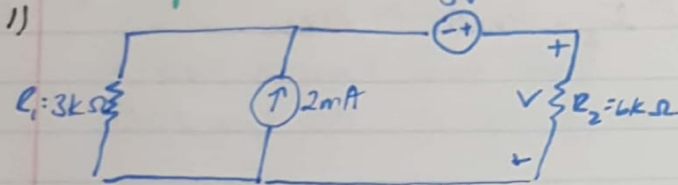


V' due to current source:

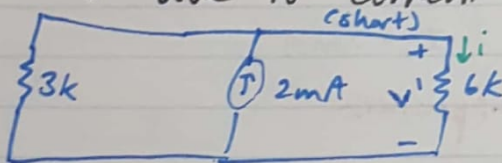

C Division:

$$i = 2\text{mA} \left(\frac{3}{3+6} \right) \text{ then } V' = R_2 i = 4\text{V}$$

V'' due to voltage source:

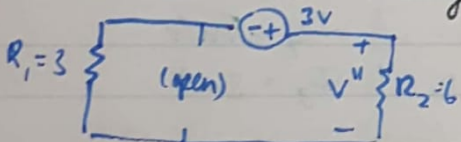


V division:


$$V'' = \frac{(3)(R_2)}{(R_1 + R_2)} = 2\text{V}$$

By superposition, $V = V' + V'' = 6\text{V}$

2)

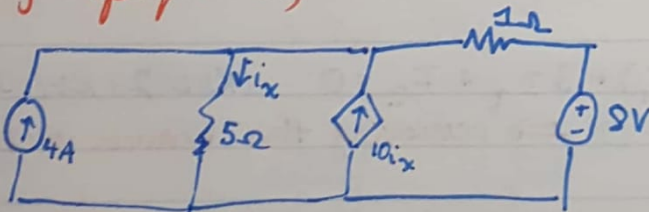


i_x' due to 4A current source:

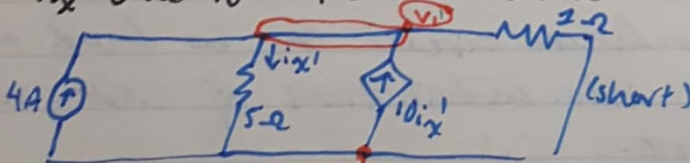

$$\text{KCL } V_1': -4 + \frac{V_1'}{5} - 10 \cdot \frac{V_1'}{5} + V_1' = 0$$

$$V_1' = -5\text{V}, i_x' = -1\text{A}$$






i_x'' due to 8V voltage source:

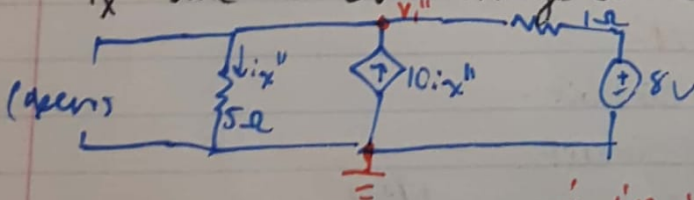

$$\text{KCL } V_1'': \frac{V_1''}{5} - 10i_x'' + \frac{V_1'' - 8}{1} = 0$$

$$V_1'' = -10\text{V}, i_x'' = -2\text{A}$$

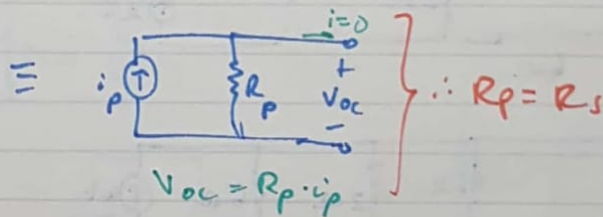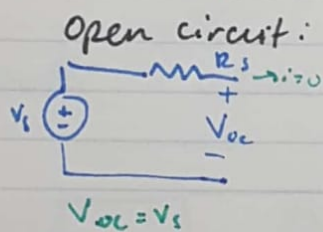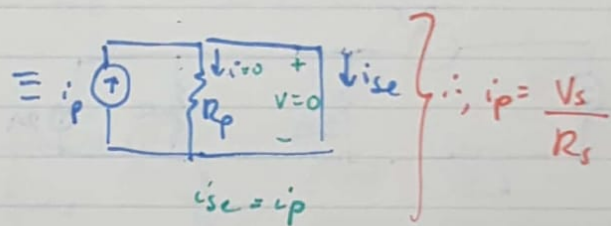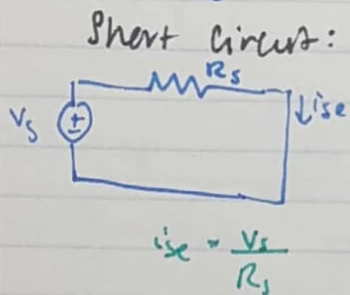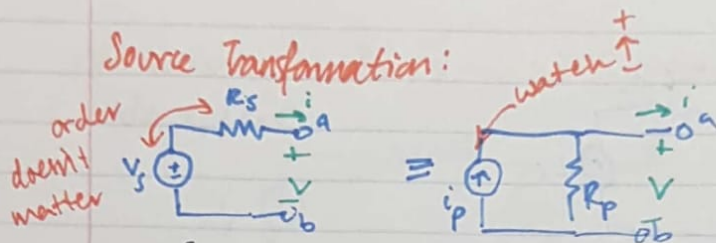
$\therefore i_x = i_x' + i_x'' = -3\text{A}$ by superposition.



unrelated

not practice

Example:

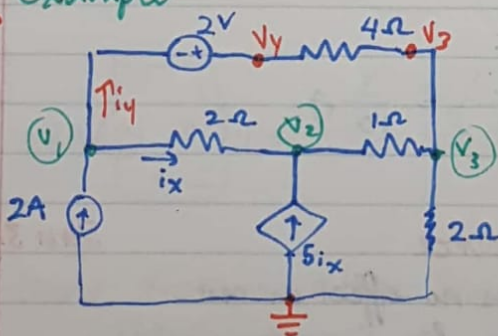






$$V_y = 2 + V_1, \quad i_x = \frac{V_1 - V_2}{2}$$

$$KCL1: -2 + \frac{V_1 - V_2}{2} + \frac{V_1 + 2 - V_3}{4} = 0$$

$$KCL2: -5i_x + V_2 - V_3 - i_x = 0$$

$$KLL3: \frac{V_3}{2} + V_3 - V_2 + \frac{V_3 - V_1 - 2}{4} = 0$$

Example:

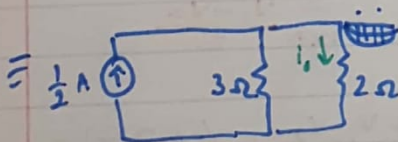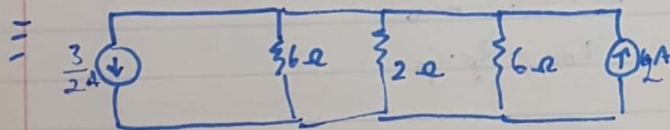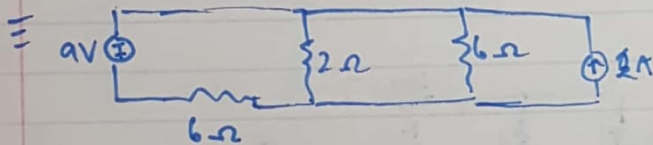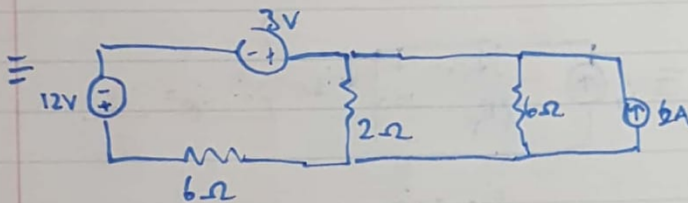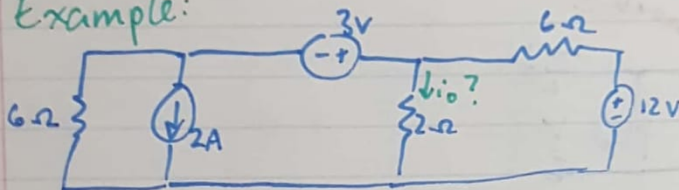


or Division:

$$i_o = \frac{1}{2} \left(\frac{3}{5} \right) = \frac{3}{10} \text{ A}$$

Resistor in parallel with Voltage source

Resistor in parallel with V source has no effect on rest.


Jan 31, 2018

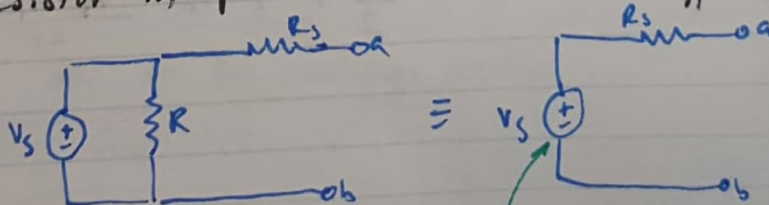


* has different current, but rest of circuit has no diff.

Resistor in Series with Current Source:

No effect

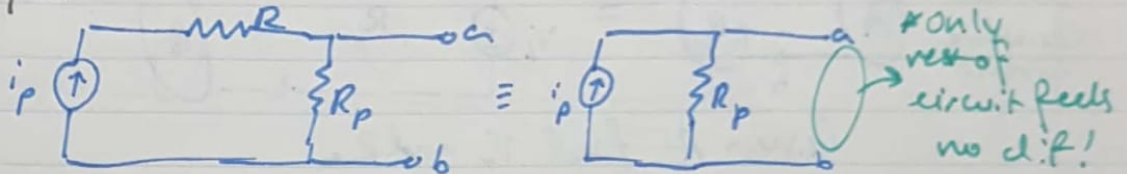


Example:

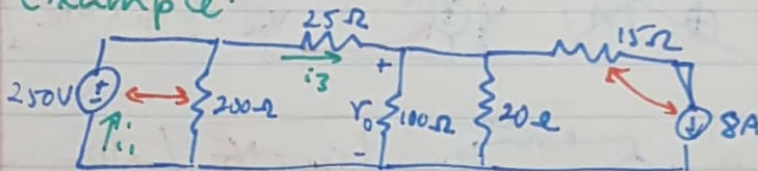


Find V_0 w

Source transformation.

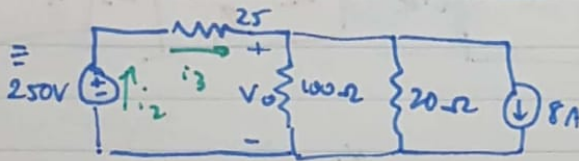


Now, source transformation.

$$i_1 \neq i_2 \text{!!!!}$$

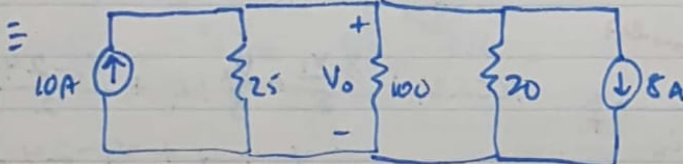

$$i_3 = \frac{250 - 20}{25}$$

$$i_1 = i_3 + \frac{250}{200}$$

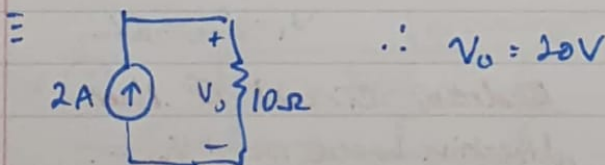


$$\therefore V_0 = 20V$$

Source Transformation Can't always be used:


→ When there's no V_{source} in series w R or C_{some} in p^{le} w R .

Thvenin Equivalent circuit:

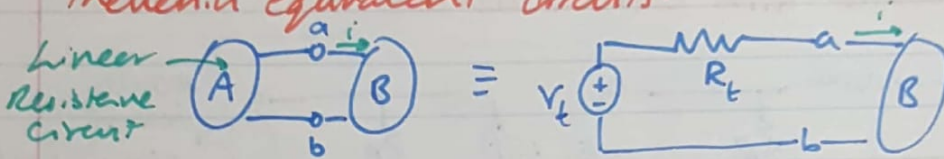


Given A, find V_t and R_t


open circuit:

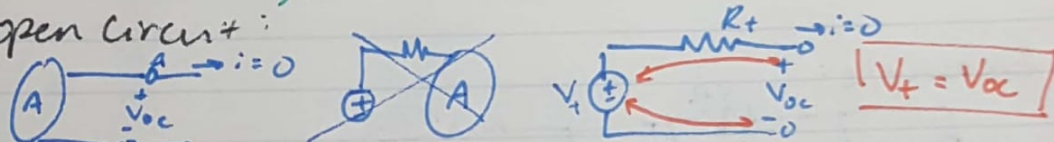

Short circuit:

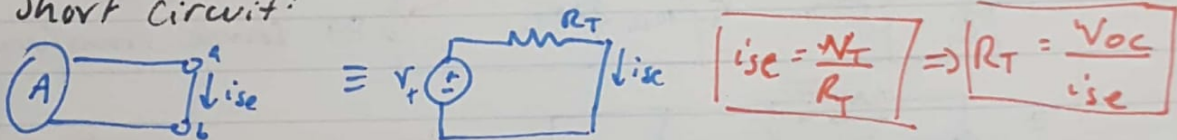

Example:

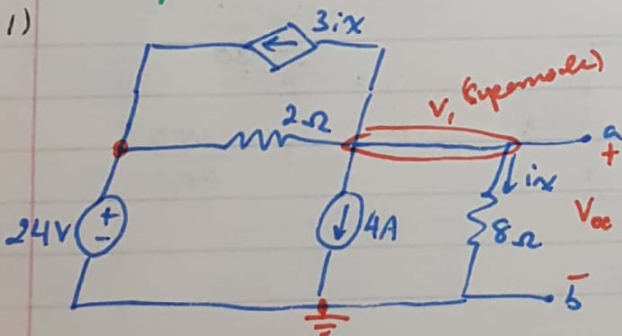

$$i_x = \frac{V_1}{8}$$


KCL V_1 :

$$\frac{3V_1}{8} + \frac{V_1}{8} + 4 + \frac{V_1 - 24}{2} = 0$$

$$\frac{1}{2}V_1 + 4 + \frac{V_1 - 24}{2} = 0$$

$$V_1 = V_{oc} = 8V$$

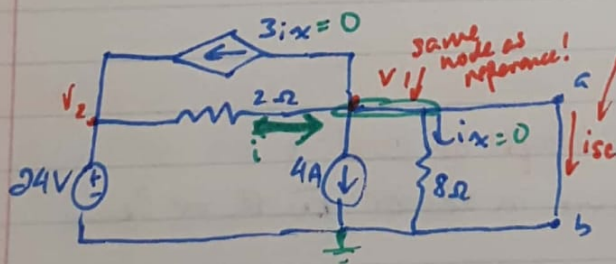
Redraw circuit in short.
direction based on $+V_{oc}$.



$$i = \frac{V_2 - V_1}{2} \text{ But } V_1 = 0 = 12A \text{ (Short)}$$


KCL \textcircled{O} : $i_{sc} = i - 4 - 0 - 0$ $i_{sc} = 8A$

Now, $R_t = 1\Omega$

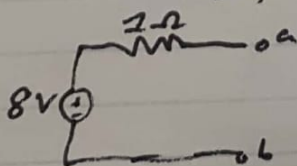


Norton Equivalent Circuit:

Feb 2, 2018.

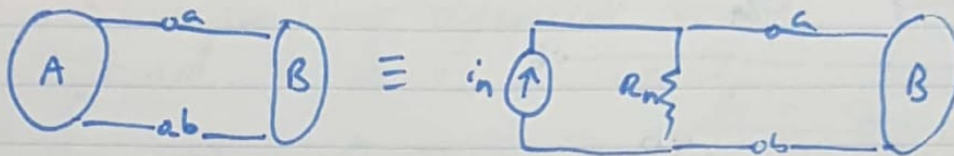


Short:

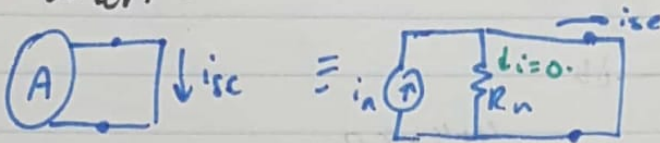

$$i_n = i_{sc}$$

Open:

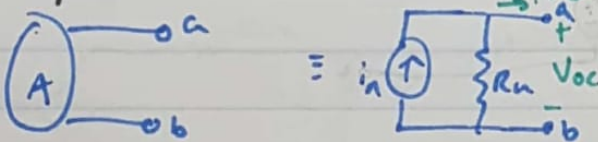


$$V_{oc} = R_n \cdot i_{sc}$$

$$R_n = \frac{V_{oc}}{i_{sc}}$$

Same as
Thev.


Example:

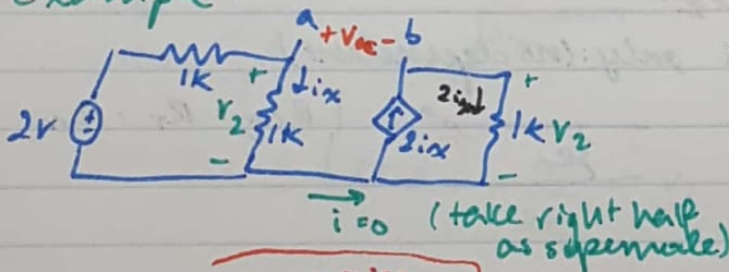

$$V_1 = \frac{(2)(1)}{(2)} = 1V \text{ (V'division)}$$

$$i_x = \frac{1V}{1K} = 1mA. \quad \therefore V_{oc} = V_1 - V_2$$

$$V_2 = (1K)(2i_x) = 2V. = -1V$$

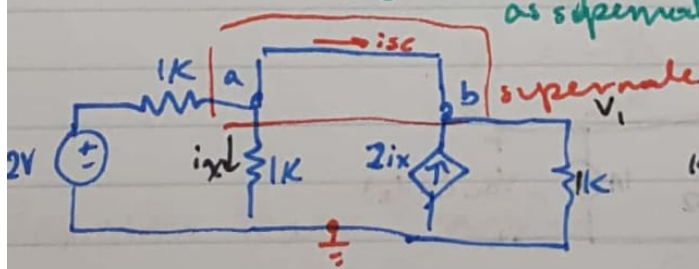


$$i_x = \frac{V_1}{1} = V_1$$

$$KCL \text{ at } V_1: \frac{V_1 - 2}{1} + \frac{V_1}{1} - 2\frac{V_1}{1} + \frac{V_1}{1} = 0$$

$$V_1 = 2V.$$

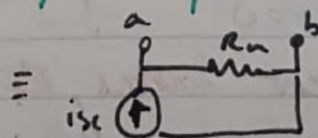
$$KCL: i_{sc} = \frac{2 - V_1}{1} - \frac{V_1}{1} = -2mA. \Rightarrow R_n = \frac{-2}{-2mA} = 1K\Omega$$




Modform:

→ up to source transformation


2)

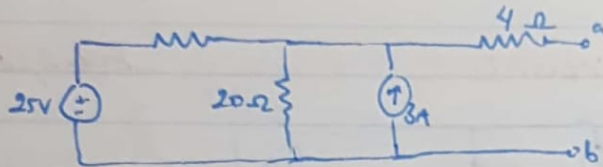

Feb 4, 2018


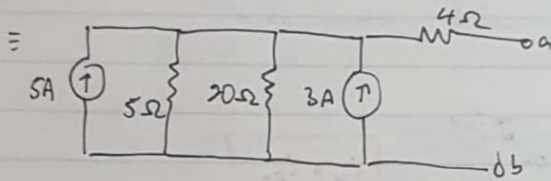


Source Transformation

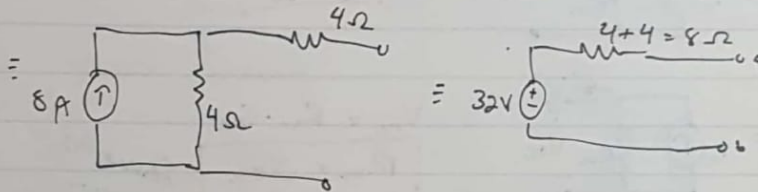

Finding R_T or R_N with R_{eq} :

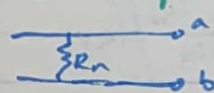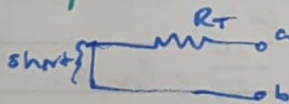
→ Independent sources only. (no dependent).



$$\left. \begin{array}{l} R_T \\ R_N \end{array} \right\} R_{eq} = R_T = R_N$$

Example:


1)

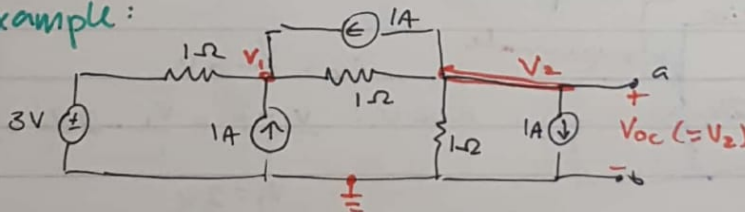


$$KCL 1: -1 - 1 + \frac{V_1 - 3}{1} + \frac{V_1 - V_2}{1} = 0 \quad \left. \begin{array}{l} V_{OC} = V_2 = \frac{1}{3} V. \end{array} \right\}$$

$$KCL 2: 1 + 1 + \frac{V_2}{1} + \frac{V_2 - V_1}{1} = 0$$

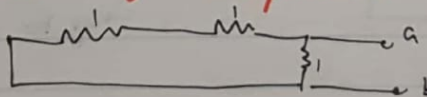Since only independent sources, $R_T = R_{eq}$. Deactivate sources.



$$R_{eq} = \frac{2}{3} \Omega$$


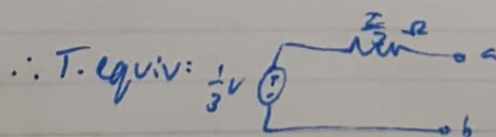


Finding R_T or R_N with External Sources:

→ Independent/dependent sources.


→ Find V_T or i_N as usual.

Can also
do $\oplus i_s$,
then find V_s

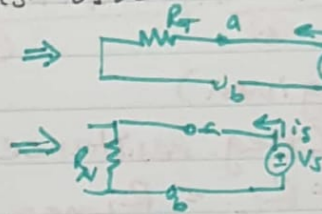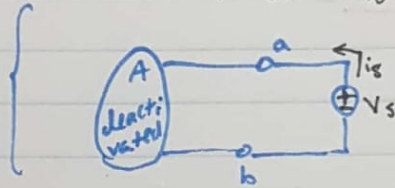


$$\left. \begin{aligned} R_T &= \frac{V_s}{i_s} \\ R_N &= \frac{V_s}{i_s} \end{aligned} \right\}$$

Example:

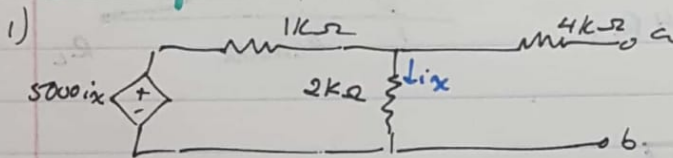

$V_{oc}, i_N = 0$ (no ind. sources)

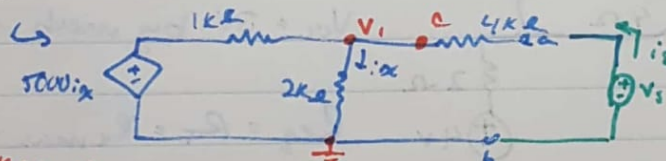


$R_T' \text{ c} \rightarrow R = 7k\Omega$

$$\text{KCL } V_1: \frac{V_1 - 5000i_x}{1k} + \frac{V_1}{2k} + \frac{V_1 - V_s}{4} = 0 \quad \left\{ \begin{aligned} \text{Sub } i_x &= \frac{V_1}{2k} \end{aligned} \right.$$

$$\Rightarrow V_1 = -\frac{V_s}{3}, \quad i_s = \frac{V_s - V_1}{4} \Rightarrow \frac{V_s}{i_s} = 3k\Omega = R_T$$

Maximum Power Transfer:

Feb 6, 2018

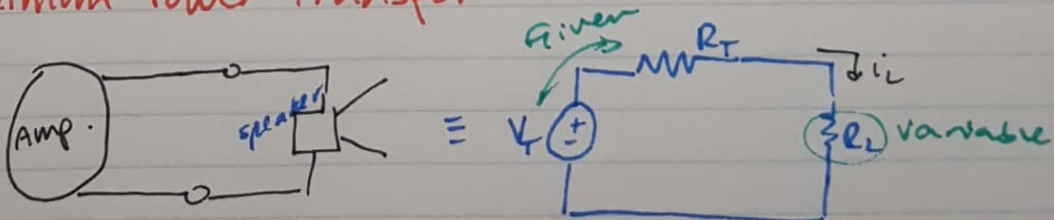

Given A, find R_L for max power

$$i_L = \frac{V_T}{R_T + R_L}$$

$$P_L = R_L \left(\frac{V_T}{R_T + R_L} \right)^2 \quad \text{R}_L \text{ variable, derive wrt } R_L.$$